

Write FSM Code

GOAL:

Build an electronic combination lock with a reset button, two number buttons (0 and 1), and an unlock output. The combination should be **01011**.



STEPS:

1. Design lock FSM (block diagram, state transitions)
2. Write Verilog module(s) for FSM

Active
Go to S