

Requirement:

Write the Verilog code for the following circuit using the least number of always blocks to describe the 3 comb clouds and the flip flops based on :-

- **Blocking & Non- Blocking concept**
- **Verilog 2001 Comb always block**

